

F2018

Q4

$$1) C + C + 2C + 4C = 8C = 2^3 C \\ = 2^k C$$

$2^k C$ series with C_b


$$\text{So } C_{eq} = \frac{2^k C_b}{2^k C + C_b} = \phi$$

$$2^k C_b = C_b + 2^k C$$

$$C_b [2^k - 1] = 2^k C$$

$$C_b = \frac{2^k}{2^k - 1} C$$

b)

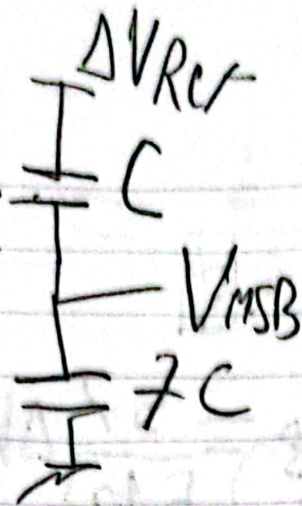


$$V_{MSB} = \frac{\Delta V_{ref} C}{7C + C}$$

$$= \Delta V_{ref} \frac{C}{8C}$$

$$= \left(\frac{1}{8} \right) V_{ref}$$


c)

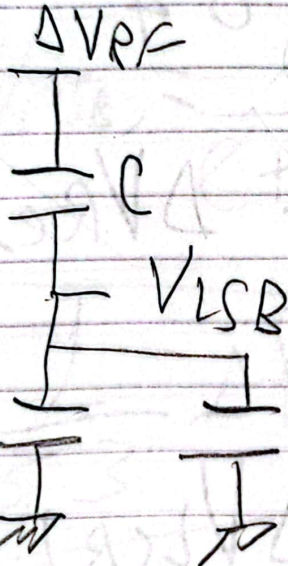

$$C_b = \frac{8}{7} C$$

$$\frac{56}{57} C = \left[\frac{C_b \times 7C}{C_b + 7C} \right]$$

↓

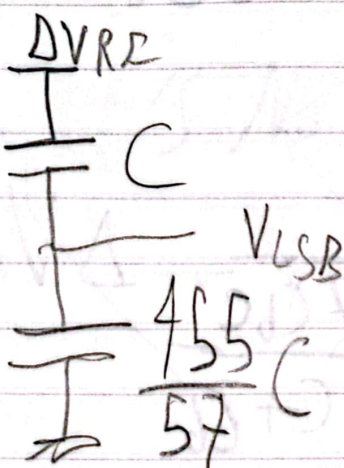

$$\Rightarrow V_{LSB} = \frac{C}{C \left[1 + \frac{455}{57} \right]} \Delta V_{ref}$$

$$\text{So if } V_{LSB} = \frac{57}{512} \Delta V_{ref}$$

$$\begin{array}{c}
 \frac{57}{512} \Delta V_{Ref} \\
 \frac{8}{7} C_b \\
 \frac{7C}{7C + \frac{8}{7}C} \Rightarrow V_{MSB} \\
 \Rightarrow V_{MSB} = \frac{57}{512} \Delta V_{Ref} \frac{8}{7C + \frac{8}{7}C} \\
 = \frac{\Delta V_{Ref}}{54} = \boxed{\frac{\Delta V_{Ref}}{25}}
 \end{array}$$

$$d) \Delta V_{MSB} = \frac{C}{7C + \frac{C_b 7C}{7C + C_b}} \Delta V_{Ref} \quad (1)$$

$$\Delta V_{MSB, LSB} = \frac{C_b}{C_b + C_{MSB}} \Delta V_{LSB}$$

$$= \frac{C_b}{C_b + 7C} \cdot \frac{C}{7C + \frac{7C_b C}{7C + C_b}} \Delta V_{Ref} \quad (2)$$

$$\frac{(2)}{(1)} \div \frac{\Delta V_{MSB, LSB}}{\Delta V_{MSB}} = \frac{C_b}{C_b + 7C}$$

$$\frac{C_b}{C_b + 7C} = \frac{1}{2^3}$$

$$2^3 C_b = C_b + 7C$$

$$7C_b = 7C \Rightarrow \boxed{C_b = C}$$

$$e) \Delta V_{MSB} = \frac{e}{C + 7C} \cdot \frac{e}{7C + \frac{7C}{2(7+1)}} \Delta V_{ref}$$

$$\Delta V_{MSB} = \frac{1}{8} \Delta V_{ref}$$

No, it's NOT Non-linear + error



Final 2019/2020

Q2

a)

Scnt linear error, as it doesn't depend on the input

Scnt Non-linear error, depends on input

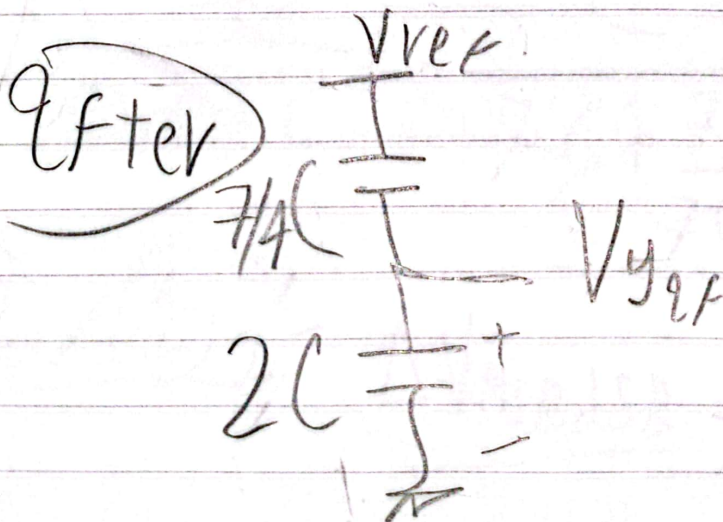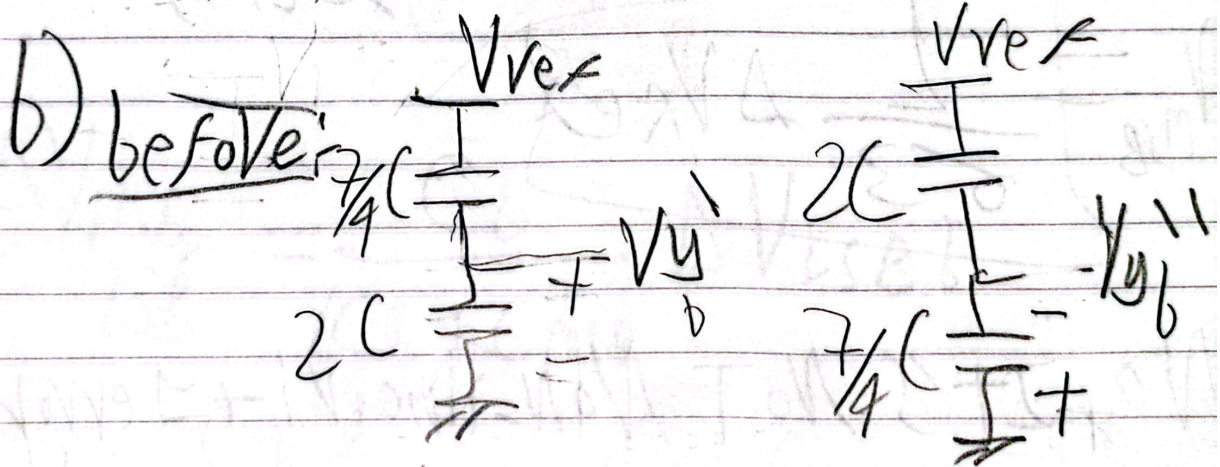

$$\Delta V_y = -V_{ref} \cdot \frac{2\cancel{x}}{\cancel{7}x + 2\cancel{x}} = -\frac{8}{15} V_{ref}$$

$$c) V_y = V_{in} - \frac{8}{15} V_{ref}$$

$$V_{in} \geq 0,5 V_{ref} \Rightarrow$$

$$V_y \geq 0,5 V_{ref} - \frac{8}{15} V_{ref}$$

$$V_y \geq \frac{-1}{30} V_{ref} \quad \therefore V_{th} \leq \frac{-1}{30} V_{ref}$$

$$d) V_{in} = 0, V_{ref} = 1,5V$$

$$ci) \Delta V_x = -\Delta V_{ref} \cdot \frac{\cancel{x}}{\cancel{x}[1+2+\frac{3}{4}]}$$

$$= \frac{-4}{15} \times \frac{3}{2} = \boxed{-0,4V}$$

$$\Delta V_y = \Delta V_x \cdot \frac{\cancel{x}}{4\cancel{x}} = \boxed{-0,2V}$$

$$(ii) \Delta V_{x_{s1}} = 2 \Delta V_{x_{s0}} = -0,8V$$

$$\left(\Delta V_{y_{s1}} = \frac{1}{4} \Delta V_{x_{s1}} = -0,2V \right)$$

$$(iii) \Delta V_{y_{s2}} = \frac{e}{3C + \frac{3eR}{4}} (-V_{ref})$$

$$= \left(-\frac{0}{7} V \right)$$

(e)

$$(i) \Delta V_x = \frac{-V_{ref} C}{\frac{25C}{4} + C} = -\frac{4}{29} V_{ref}$$

$$\Delta V_y = \frac{\Delta V_x}{4} = -\frac{1}{29} V_{ref} = -0,078V$$

$$(ii) \Delta V_y = 2 \Delta V_{y_{s0}} = -0,256 V$$

$$iii) \Delta V_y = -V_{ref} \frac{C}{3C + \frac{4C^2}{5C}} = \boxed{-0,324V}$$

f)

$$i) \Delta V_x = -V_{ref} \frac{C}{3C + \frac{4C^2}{5C}} = \boxed{-0,324V}$$

$$\Delta V_y = V_y = \frac{C}{5C} \Delta V_x = \boxed{-0,0788V}$$

ii)

$$\Delta V_x = 2 \Delta V_x = -0,788V$$

$$\Delta V_y = 2 V_y = -0,1576V$$

$$iii) \Delta V_y = -V_{ref} \frac{C}{4C + \frac{3C^2}{4C}} = -0,315V$$

$$g) V_x, \text{ as } \Delta V_x > \Delta V_y \text{ more sensitive}$$

$$DNL_x = \left(\frac{-0,2 + 0,078}{-0,1} \right) = \boxed{0,22 \text{ LSB}}$$

$$D_{NL} = - \left(\frac{-0,2 + 0,0788}{-0,2} \right)$$
$$= \boxed{0,212 \text{ LSB}}$$